



UCC

Coláiste na hOllscoile Corcaigh, Éire
University College Cork, Ireland

M.Eng.Sc Electrical and Electronic Engineering

EE4023 Digital IC Design Laboratory Project

Design of RV32I Processor for Basic Stochastic Computing

Student Name	Keerthivasan Palani
Student Number	124107157
Date	29/11/2024

Declaration:

This report was written entirely by the author, except where stated otherwise. The source of any material not created by the author has been clearly referenced. The work described in this report was conducted by the author, except where stated otherwise.

Signed: Keerthivasan Palani

Table of Contents

1. Introduction	1
2. Design Description	1
3. Module Descriptions	1
1. Instruction Fetch (IF)	1
2. Register File (RF)	1
3. Control Unit (CU)	1
4. Arithmetic Logic Unit (ALU)	1
4. Module RV32I_Processor	2
4.1 Description	2
4.2 Design Features	2
4.3 RV32I_Processor Testing (Testbench Analysis)	3
5. Module ALU	9
5.1 Description	9
5.2 Design Features	9
5.3 ALU Testing (Testbench Analysis)	10
5.4 Stochastic Computing Applications	11
6. Module InstructionFetch	16
6.1 Description	16
6.2 Design Features	17
6.3 InstructionFetch Testing (Testbench Analysis)	17
7. Module ControlUnit	22
7.1 Description	22
7.2 Design Features	22
7.3 ControlUnit Testing (Testbench Analysis)	23
8. Module RegisterFile	28
8.1 Description	28
8.2 Design Features	28
8.3 RegisterFile Testing (Testbench Analysis)	29
9. Implementation and Placement Errors	33
9.2 I/O Overutilization	33
9.2 Placement Failures	34
9.3 Overall Recommendations	34
10. Error Report and Analysis	35
11. Conclusion	35

1. Introduction

The RV32I Processor design project entails the development and simulation of a RISC-V-based 32-bit processor that adheres to the RV32I instruction set architecture. This processor supports a wide range of instructions, including arithmetic, logical, memory access, control flow, and system instructions. The aim of this project is to provide a scalable and efficient processor design suitable for educational and practical applications.

2. Design Description

The RV32I Processor is composed of several key modules, each fulfilling a specific role in the overall architecture. The primary modules include:

- **Instruction Fetch (IF):** Responsible for fetching instructions from memory and updating the program counter (PC).
- **Register File (RF):** Manages the storage and retrieval of register values used in instruction execution.
- **Control Unit (CU):** Decodes instructions and generates control signals for other modules.
- **Arithmetic Logic Unit (ALU):** Performs arithmetic and logical operations based on the instruction's opcode and function fields.

3. Module Descriptions

1. Instruction Fetch (IF)

- Inputs: clk, reset, branch_target, branch_taken, jump_taken, jump_target, interrupt_taken, interrupt_vector, stall
- Outputs: pc, instruction, exception
- Function: Fetches instructions from memory, updates the PC, and handles branching and jumping.

2. Register File (RF)

- Inputs: clk, reset, rs1, rs2, rd, write_data, reg_write
- Outputs: read_data1, read_data2
- Function: Provides storage for 32 registers and supports read and write operations.

3. Control Unit (CU)

- Inputs: opcode, funct3, funct7
- Outputs: reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump
- Function: Decodes instructions and generates control signals.

4. Arithmetic Logic Unit (ALU)

- Inputs: operand_a, operand_b, alu_control
- Outputs: alu_result, carry_out, overflow, negative, zero
- Function: Executes arithmetic and logical operations based on control signals.

4. Module RV32I_Processor

4.1 Description

The RV32I_Processor module integrates key components of the RV32I processor, including instruction fetch, register file, control unit, and ALU, to execute RISC-V instructions. This module orchestrates the interaction between these components to achieve the desired processor functionality.

4.2 Design Features

The RV32I_Processor module includes:

1. Inputs:

- clk: Clock signal.

- reset: Reset signal to initialize the processor.
- branch_target: Target address for branch instructions.
- jump_target: Target address for jump instructions.
- interrupt_taken: Signal indicating an interrupt.
- interrupt_vector: Address to jump to in case of an interrupt.
- stall: Signal to halt the processor temporarily.
- instruction_memory_input: 256-bit input representing a block of instructions from memory.

2. Outputs:

- pc: Program counter indicating the current instruction address.
- alu_result: Result of the ALU operation.
- instruction: Fetched instruction.
- reg_write: Write enable signal for the register file.
- read_data1 and read_data2: Data read from the register file.
- zero: Zero flag from the ALU.
- alu_control: ALU control signals.
- exception: Signal indicating an exceptional condition.

3. Internal Signals:

- rs1, rs2, rd: Register addresses extracted from the instruction.

4. Component Integration:

- **Instruction Fetch Module:** Fetches instructions from memory, updates the PC, and handles branches, jumps, and interrupts.
- **Register File Module:** Manages register storage and provides read and write functionality.
- **Control Unit:** Decodes instructions and generates control signals for the processor.
- **ALU:** Performs arithmetic and logical operations based on the instruction and control signals.

5. Branch and Jump Logic:

- Computes branch and jump target addresses using immediate values and the current PC.

4.3 RV32I_Processor Testing (Testbench Analysis)

The tb_RV32I_Processor module was designed to test and verify the functionality of the RV32I_Processor module. Key points from the testbench include:

1. Initialization and Configuration:

- Initializes inputs and control signals.
- Generates a clock signal.
- Applies reset to ensure the processor starts in a known state.

2. Key Test Cases:

- **Instruction Fetch:**
 - Verifies the correct fetching of instructions from memory.
- **Branch Handling:**
 - Tests the processor's ability to handle branch instructions by updating the PC to the branch target.
- **Jump Handling:**
 - Tests the processor's ability to handle jump instructions by updating the PC to the jump target.
- **Interrupt Handling:**
 - Ensures the processor correctly jumps to the interrupt vector when an interrupt is taken.
- **Stall Condition:**
 - Verifies that the PC and instruction remain stable during a stall condition.
- **Exception Detection:**

- Tests the processor's response to invalid instructions by triggering the exception signal.


3. Sample Outputs:

- **Instruction Fetch:**
 - Correct instructions are fetched based on the current PC.
- **Branch Handling:**
 - PC updates to the branch target when a branch is taken.
- **Jump Handling:**
 - PC updates to the jump target when a jump is taken.
- **Interrupt Handling:**
 - PC updates to the interrupt vector when an interrupt is taken.
- **Stall Condition:**
 - PC and instruction remain stable during a stall.
- **Exception Detection:**
 - Exception signal is triggered for invalid instructions.


4. Results and Observations:

- The processor correctly handled all test cases, including instruction fetch, branch, jump, interrupt, stall, and exception conditions.
- The integrated components (Instruction Fetch, Register File, Control Unit, ALU) worked seamlessly to execute instructions.
- Control signals and data paths were correctly managed, ensuring accurate instruction execution.
- The processor demonstrated robust performance under various conditions, including handling exceptional scenarios.



Simulation Waveform

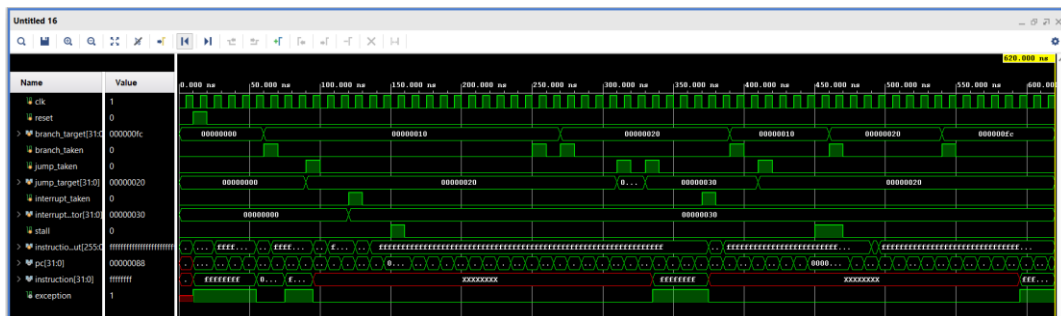

Synthesized Design

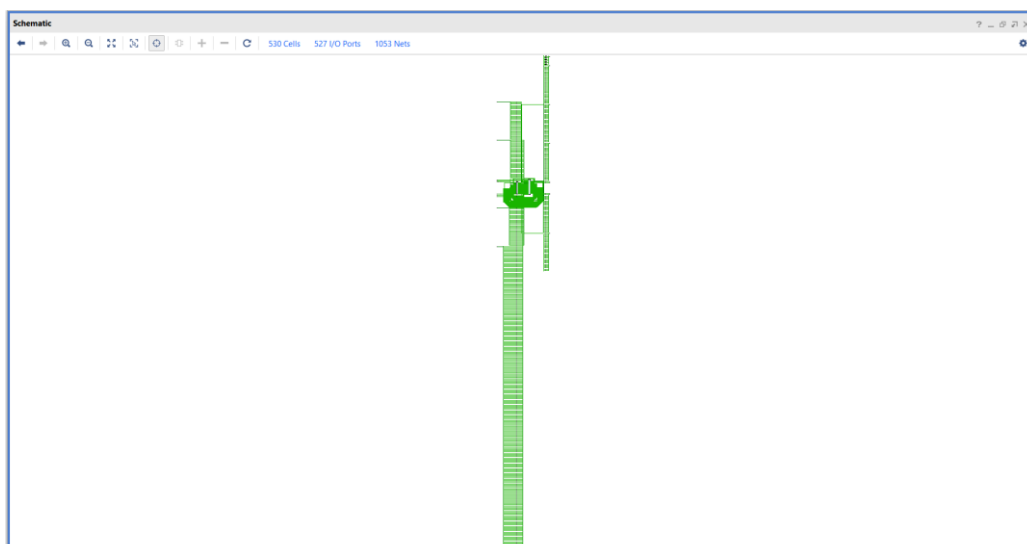

Elaborated Design

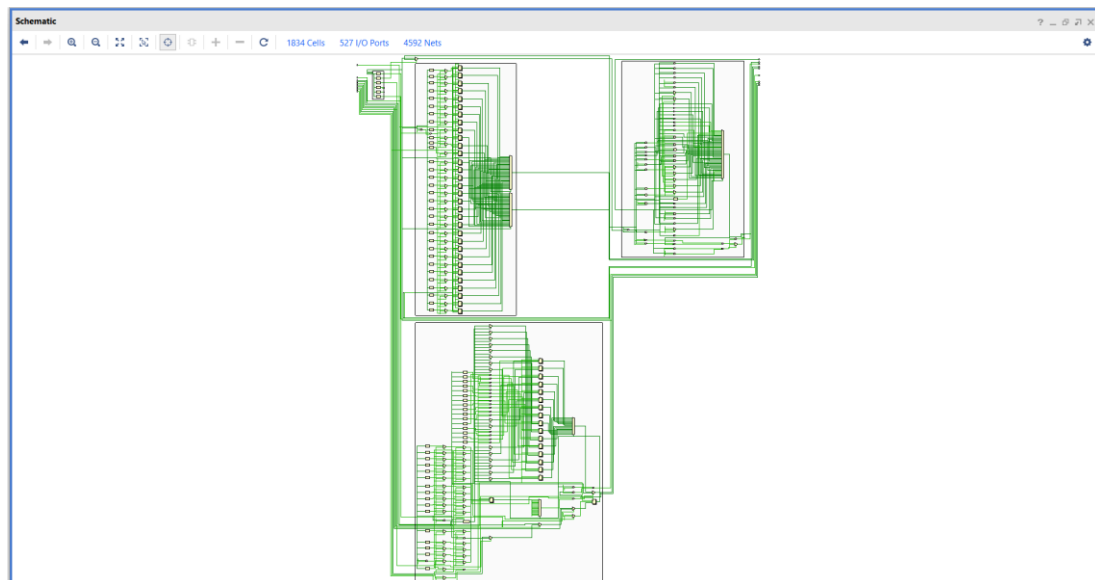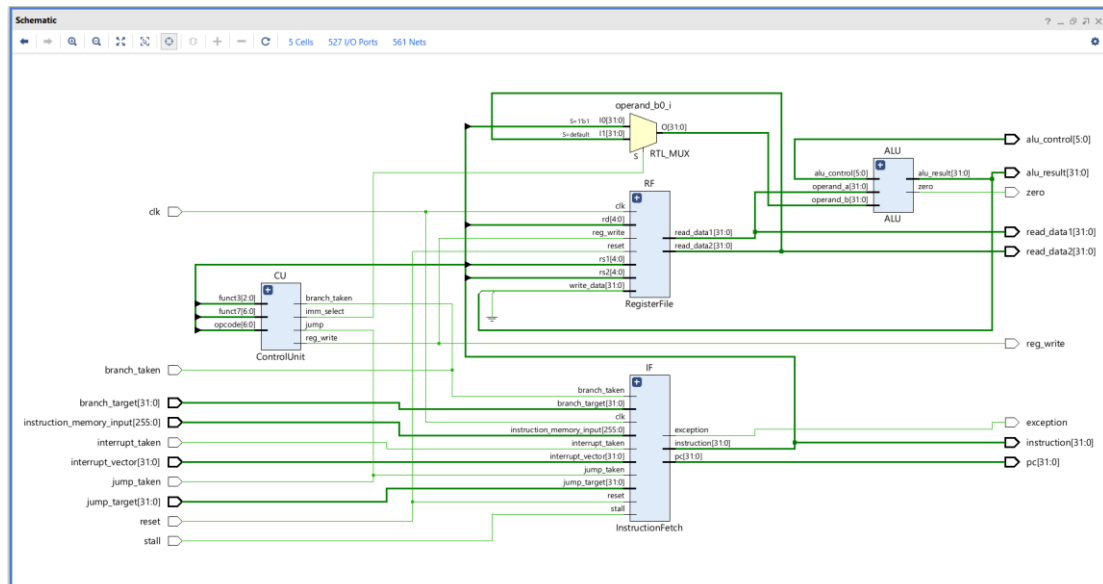

Verilog Code

RV32I_Processor.v

D:/Vivado/RISC_1/RISC_1.srcs/sources_1/new/RV32I_Processor.v

```
23 module RV32I_Processor (
24     input clk,
25     input reset,
26     input [31:0] branch_target,
27     //input branch_taken,          // Correctly declared as input port
28     //input jump_taken,           // Correctly declared as input port
29     input [31:0] jump_target,
30     input interrupt_taken,
31     input [31:0] interrupt_vector,
32     input stall,
33     input [255:0] instruction_memory_input, // Instruction memory input port
34     // Outputs
35     output [31:0] pc,
36     output [31:0] alu_result,
37     output wire [31:0] instruction,
38     output reg_write,
39     // Outputs for register file and ALU debug
40     output [31:0] read_data1,
41     output [31:0] read_data2,
42     output zero,
43     output [5:0] alu_control,
44     output exception
45 );
46
47 // Internal signals for InstructionFetch and control signals
48 wire [31:0] branch_target_wire, jump_target_wire, interrupt_vector_wire;
49 wire stall_wire, interrupt_taken_wire;
50
51 // Assign fields from instruction (this is part of the instruction decoding)
52 wire [4:0] rs1, rs2, rd;
53 assign rs1 = instruction[19:15];
54 assign rs2 = instruction[24:20];
55 assign rd = instruction[11:7];
56
57 // Instruction Fetch Module instantiation
58 InstructionFetch IF (
59     .clk(clk),
60     .reset(reset),
61     .branch_target(branch_target), // Connect to the top-level port
62     .branch_taken(CU_branch_taken), // Use the branch_taken input port directly
63     .jump_taken(CU_jump_taken), // Use the jump_taken input port directly
64     .jump_target(jump_target), // Connect to the top-level port
65     .interrupt_taken(interrupt_taken), // Connect to the top-level port
66     .interrupt_vector(interrupt_vector), // Connect to the top-level port
67     .stall(stall), // Connect to the top-level port
68     .instruction_memory_input(instruction_memory_input),
69     .pc(pc),
70     .instruction(instruction), // Instruction driven by IF module
71     .exception(exception)
72 );
73
74 // Register File Module instantiation
75 RegisterFile RF (
76     .clk(clk),
77     .reset(reset),
78     .rs1(rs1),
79     .rs2(rs2),
80     .rd(rd),
81     .write_data(write_data),
82     .reg_write(reg_write),
83     .read_data1(read_data1),
84     .read_data2(CU_data2)
85 );
86
87 // Control Unit instantiation
88 ControlUnit CU (
89     .opcode(instruction[6:0]),
90     .funct3(instruction[14:12]),
91     .funct7(instruction[31:25]),
92     .reg_write(reg_write),
93     .mem_read(mem_read),
94     .mem_write(mem_write),
95     .mem_to_reg(mem_to_reg),
96     .branch_taken(branch_taken),
97     .imm_select(imm_select),
98     .jump(jump_taken) // Directly use the jump_taken input port
99 );
100
101 // ALU instantiation
102 ALU ALU (
103     .operand_a(read_data1),
```

```

81     .write_data(write_data),
82     .reg_write(reg_write),
83     .read_data1(read_data1),
84     .read_data2(read_data2)
85 );
86
87 // Control Unit instantiation
88 ControlUnit CU (
89     .opcode(instruction[6:0]),
90     .funct3(instruction[14:12]),
91     .funct7(instruction[31:25]),
92     .reg_write(reg_write),
93     .mem_read(mem_read),
94     .mem_write(mem_write),
95     .mem_to_reg(mem_to_reg),
96     .branch_taken(branch_taken),
97     .imm_select(imm_select),
98     .jump(jump_taken) // Directly use the jump_taken input port
99 );
100
101 // ALU instantiation
102 ALU ALU (
103     .operand_a(read_data1),
104     .operand_b(imm_select ? ({20(instruction[31])}, instruction[31:20]) : read_data2),
105     .alu_control(alu_control),
106     .alu_result(alu_result),
107     .carry_out(),
108     .overflow(),
109     .negative(),
110     .zero(zero)
111 );
112
113 // Write Data Assignment (select data from memory or ALU result)
114 assign write_data = mem_to_reg ? alu_result : alu_result; // In a real processor, this would also include memory data if mem_to_reg is set
115
116 // Branch Target and Jump Target Logic
117 assign branch_target_wire = pc + ({19(instruction[31])}, instruction[31], instruction[7], instruction[30:25], instruction[11:8], 1'b0); // Branch offset
118 assign jump_target_wire = pc + ({11(instruction[31])}, instruction[31], instruction[19:12], instruction[20], instruction[30:21], 1'b0); // Jump offset
119
120 endmodule
121

```

TB_RV32I_Processor.v

```

22 module tb_RV32I_Processor;
23
24     reg clk;
25     reg reset;
26     reg [31:0] branch_target;
27     reg branch_taken;
28     reg jump_taken;
29     reg [31:0] jump_target;
30     reg interrupt_taken;
31     reg [31:0] interrupt_vector;
32     reg stall;
33     reg [255:0] instruction_memory_input;
34
35     wire [31:0] pc;
36     wire [31:0] instruction;
37     wire exception;
38     wire branch_taken;
39     wire jump_taken;
40
41     RV32I_Processor uut (
42         .clk(clk),
43         .reset(reset),
44         .branch_target(branch_target),
45         // .branch_taken(branch_taken),
46         // .jump_taken(jump_taken),
47         .jump_target(jump_target),
48         .interrupt_taken(interrupt_taken),
49         .interrupt_vector(interrupt_vector),
50         .stall(stall),
51         .instruction_memory_input(instruction_memory_input),
52         .pc(pc),
53         .instruction(instruction),
54         .exception(exception)
55     );
56     // Clock generation
57     always #5 clk = ~clk;
58     // Generate instruction memory data dynamically based on PC
59     always @(pc) begin
60         case (pc[7:0]) // Simulate a 256-byte instruction memory
61             8'h00: instruction_memory_input = {32'h00000033, 32'h00010063, 32'h0000006F, 32'hFFFFFFF}; // Block 0
62             8'h10: instruction_memory_input = {32'h12345678, 32'h9ABCDEF0, 32'h00000011, 32'h22222222}; // Block 0

```



```

63      8'h20: instruction_memory_input = {32'h33333333, 32'h44444444, 32'h55555555, 32'h66666666}; // Block 2
64      8'h30: instruction_memory_input = {32'h77777777, 32'h88888888, 32'h99999999, 32'hAAAAAAA}; // Block 3
65      default: instruction_memory_input = {8{32'hFFFFFF}}; // Default invalid data
66  endcase
67  end
68  // Test cases
69  initial begin
70      $monitor("Time: %0t | PC: %h | Instruction: %h | Exception: %b",
71              $time, pc, instruction, exception);
72      // Initialize signals
73      clk = 0;
74      reset = 0;
75      branch_target = 0;
76      branch_taken = 0;
77      jump_taken = 0;
78      jump_target = 0;
79      interrupt_taken = 0;
80      interrupt_vector = 0;
81      stall = 0;
82      instruction_memory_input = 256'b0;
83      // Apply reset
84      #10 reset = 1;
85      #10 reset = 0;
86      // Test instruction fetch
87      #40;
88      // Basic Branch test
89      branch_taken = 1; branch_target = 32'h10; #10 branch_taken = 0;
90      #20;
91      // Basic Jump test
92      jump_taken = 1; jump_target = 32'h20; #10 jump_taken = 0;
93      #20;
94      // Interrupt test
95      interrupt_taken = 1; interrupt_vector = 32'h30; #10 interrupt_taken = 0;
96      #20;
97      // Stall test
98      stall = 1; #10 stall = 0;
99      #20;
100     // Exception test
101     #50 instruction_memory_input = {8{32'hFFFFFF}};
102     #20;
103     // ** Additional Test Cases **
104     // 1. Back-to-back branches
105     branch_taken = 1; branch_target = 32'h10; #10 branch_taken = 0;
106     #10 branch_taken = 1; branch_target = 32'h20; #10 branch_taken = 0;
107     #30;
108     // 2. Nested jump test (jump followed by another jump)
109     jump_taken = 1; jump_target = 32'h10; #10 jump_taken = 0;
110     #10 jump_taken = 1; jump_target = 32'h30; #10 jump_taken = 0;
111     #30;
112     // 3. Interrupt with branch and jump
113     interrupt_taken = 1; interrupt_vector = 32'h30; #10 interrupt_taken = 0;
114     #10 branch_taken = 1; branch_target = 32'h10; #10 branch_taken = 0;
115     #10 jump_taken = 1; jump_target = 32'h20; #10 jump_taken = 0;
116     #30;
117     // 4. Combined stall and branch
118     stall = 1; #10;
119     branch_taken = 1; branch_target = 32'h20; #10 branch_taken = 0;
120     stall = 0; #20;
121     // 5. Instruction memory full of valid data
122     instruction_memory_input = {32'h12345678, 32'h87654321, 32'hFEDCBA98, 32'hABCDEF01,
123                               32'h55555555, 32'hAAAAAAA, 32'h11111111, 32'h22222222};
124     #50;
125     // 6. PC wrap-around (boundary conditions)
126     branch_taken = 1; branch_target = 32'hFC; #10 branch_taken = 0; // Near the end of memory
127     #20;
128     // Finish simulation
129     #50 $finish;
130  end
131 endmodule

```

5. Module ALU

5.1 Description

The Arithmetic Logic Unit (ALU) is a core component of the RV32I processor, performing arithmetic, logical, shift, and stochastic operations. The ALU designed here has an extended operation set with **6-bit control signals**, enabling versatile functionality, including arithmetic, logical, and specialized stochastic computing operations. This design ensures compatibility with both standard RV32I instructions and additional custom operations for stochastic computing.

5.2 Design Features

The ALU module includes:

1. Arithmetic Operations:

- Basic operations like addition, subtraction, multiplication, and division.
- Additional operations such as modulo, increment, decrement, and negation.

2. Logical Operations:

- Standard bitwise operations (AND, OR, XOR, NOT).
- Extended operations such as NAND, NOR, XNOR, bit clear, parity, and reduce OR.

3. Shift and Rotate Operations:

- Logical shifts (SLL, SRL), arithmetic shift right (SRA), and rotate operations (ROL, ROR).
- Circular shifts for flexible data manipulation.

4. Comparison Operations:

- Equal, less-than, greater-than, and similar comparisons for decision-making instructions.

5. Stochastic Computing Support:

- Operations for probabilistic systems, such as AND-based probability computation and random number generation.

6. Overflow, Negative, and Zero Flag Detection:

- Overflow detection for signed addition/subtraction.
- Negative flag to indicate if the result is negative.
- Zero flag to indicate when the result is zero.

7. Extended Specialized Features:

- Cryptographic primitive operations like XOR-based Gray code and bit selection.
- Support for floating-point approximations and scaling.

5.3 ALU Testing (Testbench Analysis)

The tb_ALU module was designed to test and verify the functionality of the ALU. Key points from the testbench include:

1. Initialization and Configuration:

- The testbench initializes the operands and control signals.
- A sequence of test cases evaluates different ALU operations.

2. Key Test Cases:

○ Arithmetic Operations:

- Addition (ADD): Verified accurate sum results and flag updates.
- Subtraction (SUB): Checked for correct difference and signed behaviour.
- Multiplication (MUL) and Division (DIV): Validated accurate product and quotient outputs.

○ Logical Operations:

- AND, OR, and XOR were tested for standard truth table behaviour.
- NOT and bitwise clear operations demonstrated correct bitwise inversion and masking.
- **Shift and Rotate:**
 - Logical (SLL, SRL) and arithmetic (SRA) shifts tested for proper handling of sign and data.
 - Rotate (ROL, ROR) operations verified correct bit rotation.
- **Comparison and Conditional Flags:**
 - Comparison results (e.g., greater-than, less-than) validated against expected conditions.
 - Flag outputs (zero, overflow, negative) verified correct updates based on results.
- **Stochastic and Random Operations:**
 - Verified random number generation and probabilistic logic (AND/OR reduction).
 - Demonstrated the capability of stochastic computing for specialized applications.

3. Sample Outputs:

- **ADD Operation (5 + 3):** Result: 8, Zero: 0, Overflow: 0, Negative: 0.
- **SUB Operation (16- 5):** Result: 11, Zero: 0, Overflow: 0, Negative: 0.
- **MUL Operation (5 * 4):** Result: 20, Zero: 0, Overflow: 0, Negative: 0.
- **XOR Operation (5 ^ 3):** Result: 6, Zero: 0, Overflow: 0, Negative: 0.
- **RANDOM Operation:** Result: Random 32-bit value, verifying stochastic behaviour.

4. Results and Observations:

- All operations produced expected results under normal conditions.
- Overflow, zero, and negative flags were triggered as appropriate.
- Stochastic operations demonstrated compatibility with probabilistic systems, with random number generation producing varying outputs across test runs.

5.4 Stochastic Computing Applications

The ALU design supports basic stochastic computing, crucial for systems requiring probabilistic operations. Examples include:

- **Random Number Generation:** Useful for simulations, cryptographic algorithms, and machine learning.
- **Probabilistic Logic (AND/OR):** Computes probabilities using stochastic encoding, applicable in neural networks and decision-making systems.

Verilog code

```

ALU.v
D:/Vivado/RISC_1/RISC_1srcs/sources_1/new/ALU.v

23 module ALU (
24     input [31:0] operand_a,
25     input [31:0] operand_b,
26     input [5:0] alu_control, // Extended control to 6 bits for more operations
27     output reg [31:0] alu_result,
28     output reg carry_out,
29     output reg overflow,
30     output reg negative,
31     output zero
32 );
33
34 assign zero = (alu_result == 0);
35
36 always @(*) begin
37     // Default flag values
38     carry_out = 0;
39     overflow = 0;
40     negative = 0;
41
42     case (alu_control)
43         // Arithmetic Operations
44         6'b000000: alu_result = operand_a + operand_b; // ADD
45         6'b000001: alu_result = operand_a - operand_b; // SUB
46         6'b000010: alu_result = operand_a * operand_b; // MUL
47         6'b000011: alu_result = operand_a / operand_b; // DIV
48         6'b000100: alu_result = operand_a % operand_b; // MOD
49         6'b000101: alu_result = ~operand_a; // NEG
50         6'b000110: alu_result = operand_a + 1; // INC
51         6'b000111: alu_result = operand_a - 1; // DEC
52         6'b001000: alu_result = operand_a ** operand_b; // EXP
53         6'b001001: alu_result = (operand_a < operand_b) ? operand_a : operand_b; // MIN
54         6'b001010: alu_result = (operand_a > operand_b) ? operand_a : operand_b; // MAX
55
56         // Logical Operations
57         6'b010000: alu_result = operand_a & operand_b; // AND
58         6'b010001: alu_result = operand_a | operand_b; // OR
59         6'b010010: alu_result = operand_a ^ operand_b; // XOR
60         6'b010011: alu_result = ~(operand_a & operand_b); // NAND
61         6'b010100: alu_result = ~(operand_a | operand_b); // NOR
62         6'b010101: alu_result = ~(operand_a ^ operand_b); // XNOR
63         6'b010110: alu_result = ~operand_a; // NOT

```

```

64      6'b010111: alu_result = operand_a & ~operand_b;          // BIT CLEAR
65      6'b011000: alu_result = |operand_a;                     // REDUCE OR
66      6'b011001: alu_result = ^operand_a;                     // PARITY
67      6'b011010: alu_result = (operand_a != 0) ? 32'hFFFFFF : 0; // ALL 1s if non-zero
68
69      // Shift and Rotate Operations
70      6'b100000: alu_result = operand_a << operand_b[4:0];     // SLL
71      6'b100001: alu_result = operand_a >> operand_b[4:0];     // SRL
72      6'b100010: alu_result = $signed(operand_a) >>> operand_b[4:0]; // SRA
73      6'b100011: alu_result = {operand_a[30:0], operand_a[31]}; // ROL
74      6'b100100: alu_result = {operand_a[0], operand_a[31:1]}; // ROR
75      6'b100101: alu_result = operand_a << (32 - operand_b);   // CIRCULAR LEFT SHIFT
76      6'b100110: alu_result = operand_a >> (32 - operand_b);   // CIRCULAR RIGHT SHIFT
77
78      // Comparison Operations
79      6'b101000: alu_result = (operand_a == operand_b) ? 1 : 0; // EQUAL
80      6'b101001: alu_result = (operand_a < operand_b) ? 1 : 0; // LESS THAN
81      6'b101010: alu_result = (operand_a > operand_b) ? 1 : 0; // GREATER THAN
82      6'b101011: alu_result = (operand_a <= operand_b) ? 1 : 0; // LESS THAN OR EQUAL
83      6'b101100: alu_result = (operand_a >= operand_b) ? 1 : 0; // GREATER THAN OR EQUAL
84
85      // Cryptographic and Specialized Operations
86      6'b110000: alu_result = operand_a ^ operand_b;          // XOR (Cryptographic Primitive)
87      6'b110001: alu_result = ~operand_a;                     // BITWISE NOT
88      6'b110010: alu_result = operand_a[operand_b[4:0]];       // BIT SELECT
89      6'b110011: alu_result = {operand_a, operand_b};          // CONCATENATION
90      6'b110100: alu_result = operand_a ^ (operand_a >> 1);    // GRAY CODE
91
92      // Floating-Point Operations (Pseudo-Support via Integer Approximation)
93      6'b111000: alu_result = operand_a * operand_a;          // SQUARE
94      6'b111001: alu_result = operand_a / 2;                   // APPROXIMATE DIVISION BY 2
95      6'b111010: alu_result = operand_a * operand_b / 1000;    // APPROX MULTIPLY-SCALE
96
97      // Stochastic Computing Operations
98      6'b111100: alu_result = (operand_a & operand_b) ? 32'h1 : 0; // AND Probability
99      6'b111101: alu_result = operand_a | operand_b;          // OR Probability
100     6'b111110: alu_result = ^ (operand_a & operand_b);       // XOR Reduce for Randomness
101     6'b111111: alu_result = $random;                          // RANDOM Number Generation
102
103     // Default case
104     default: alu_result = 32'b0;
105
106
107
108
109
110
111
112
113
114
115
116

```

```

76      6'b100110: alu_result = operand_a >> (32 - operand_b);   // CIRCULAR RIGHT SHIFT
77
78      // Comparison Operations
79      6'b101000: alu_result = (operand_a == operand_b) ? 1 : 0; // EQUAL
80      6'b101001: alu_result = (operand_a < operand_b) ? 1 : 0; // LESS THAN
81      6'b101010: alu_result = (operand_a > operand_b) ? 1 : 0; // GREATER THAN
82      6'b101011: alu_result = (operand_a <= operand_b) ? 1 : 0; // LESS THAN OR EQUAL
83      6'b101100: alu_result = (operand_a >= operand_b) ? 1 : 0; // GREATER THAN OR EQUAL
84
85      // Cryptographic and Specialized Operations
86      6'b110000: alu_result = operand_a ^ operand_b;          // XOR (Cryptographic Primitive)
87      6'b110001: alu_result = ~operand_a;                     // BITWISE NOT
88      6'b110010: alu_result = operand_a[operand_b[4:0]];       // BIT SELECT
89      6'b110011: alu_result = {operand_a, operand_b};          // CONCATENATION
90      6'b110100: alu_result = operand_a ^ (operand_a >> 1);    // GRAY CODE
91
92      // Floating-Point Operations (Pseudo-Support via Integer Approximation)
93      6'b111000: alu_result = operand_a * operand_a;          // SQUARE
94      6'b111001: alu_result = operand_a / 2;                   // APPROXIMATE DIVISION BY 2
95      6'b111010: alu_result = operand_a * operand_b / 1000;    // APPROX MULTIPLY-SCALE
96
97      // Stochastic Computing Operations
98      6'b111100: alu_result = (operand_a & operand_b) ? 32'h1 : 0; // AND Probability
99      6'b111101: alu_result = operand_a | operand_b;          // OR Probability
100     6'b111110: alu_result = ^ (operand_a & operand_b);       // XOR Reduce for Randomness
101     6'b111111: alu_result = $random;                          // RANDOM Number Generation
102
103     // Default case
104     default: alu_result = 32'b0;
105
106     endcase
107
108     // Overflow Detection
109     if (alu_control == 6'b000000 || alu_control == 6'b000001) begin
110         overflow = (~operand_a[31] & ~operand_b[31] & alu_result[31]) |
111             (operand_a[31] & operand_b[31] & ~alu_result[31]);
112     end
113
114     // Negative Detection
115     negative = alu_result[31];
116
117 endmodule

```

Testbench Code

tb_ALU.v

D:/Vivado/RISC_1/RISC_1.srscs/sources_1/new/tb_ALU.v

```
22 module tb_ALU;
23
24     // Inputs
25     reg [31:0] operand_a;
26     reg [31:0] operand_b;
27     reg [5:0] alu_control;
28
29     // Outputs
30     wire [31:0] alu_result;
31     wire carry_out;
32     wire overflow;
33     wire negative;
34     wire zero;
35
36     // Instantiate the ALU module
37     ALU uut (
38         .operand_a(operand_a),
39         .operand_b(operand_b),
40         .alu_control(alu_control),
41         .alu_result(alu_result),
42         .carry_out(carry_out),
43         .overflow(overflow),
44         .negative(negative),
45         .zero(zero)
46     );
47
48     initial begin
49         // Initialize inputs
50         operand_a = 32'b0;
51         operand_b = 32'b0;
52         alu_control = 6'b000000; // ADD operation
53
54         // Test cases
55         $display("Starting ALU Testbench");
56
57         // Test ADD operation
58         #10;
59         operand_a = 32'h00000005;
60         operand_b = 32'h00000003;
61         alu_control = 6'b000000; // ADD
62         #10;
63
64         $display("ADD: 5 + 3 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
65             operand_a, alu_result, zero, overflow, negative, carry_out);
66
67         // Test SUB operation
68         #10;
69         operand_a = 32'h00000010;
70         operand_b = 32'h00000005;
71         alu_control = 6'b000001; // SUB
72         #10;
73         $display("SUB: 16 - 5 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
74             operand_a, alu_result, zero, overflow, negative, carry_out);
75
76         // Test MUL operation
77         #10;
78         operand_a = 32'h00000005;
79         operand_b = 32'h00000004;
80         alu_control = 6'b000010; // MUL
81         #10;
82         $display("MUL: 5 * 4 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
83             operand_a, alu_result, zero, overflow, negative, carry_out);
84
85         // Test DIV operation
86         #10;
87         operand_a = 32'h00000010;
88         operand_b = 32'h00000002;
89         alu_control = 6'b000011; // DIV
90         #10;
91         $display("DIV: 16 / 2 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
92             operand_a, alu_result, zero, overflow, negative, carry_out);
93
94         // Test MOD operation
95         #10;
96         operand_a = 32'h00000010;
97         operand_b = 32'h00000003;
98         alu_control = 6'b000100; // MOD
99         #10;
100        $display("MOD: 16 %% 3 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
101            operand_a, alu_result, zero, overflow, negative, carry_out);
102
103        // Test NEG operation
104        #10;
```

```

103     #10;
104     operand_a = 32'h00000005;
105     alu_control = 6'b000101; // NEG
106     #10;
107     $display("NEG: -5 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
108             operand_a, alu_result, zero, overflow, negative, carry_out);
109
110     // Test INC operation
111     #10;
112     operand_a = 32'h00000005;
113     alu_control = 6'b000110; // INC
114     #10;
115     $display("INC: 5 + 1 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
116             operand_a, alu_result, zero, overflow, negative, carry_out);
117
118     // Test DEC operation
119     #10;
120     operand_a = 32'h00000005;
121     alu_control = 6'b000111; // DEC
122     #10;
123     $display("DEC: 5 - 1 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
124             operand_a, alu_result, zero, overflow, negative, carry_out);
125
126     // Test AND operation
127     #10;
128     operand_a = 32'h00000005;
129     operand_b = 32'h00000003;
130     alu_control = 6'b010000; // AND
131     #10;
132     $display("AND: 5 & 3 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
133             operand_a, alu_result, zero, overflow, negative, carry_out);
134
135     // Test OR operation
136     #10;
137     operand_a = 32'h00000005;
138     operand_b = 32'h00000003;
139     alu_control = 6'b010001; // OR
140     #10;
141     $display("OR: 5 | 3 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
142             operand_a, alu_result, zero, overflow, negative, carry_out);
143
144     // Test XOR operation
145     #10;
146     operand_a = 32'h00000005;
147     operand_b = 32'h00000003;
148     alu_control = 6'b010010; // XOR
149     #10;
150     $display("XOR: 5 ^ 3 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
151             operand_a, alu_result, zero, overflow, negative, carry_out);
152
153     // Test SLL (Shift Left Logical)
154     #10;
155     operand_a = 32'h00000001;
156     operand_b = 32'h00000002; // Shift by 2
157     alu_control = 6'b100000; // SLL
158     #10;
159     $display("SLL: 1 << 2 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
160             operand_a, alu_result, zero, overflow, negative, carry_out);
161
162     // Test SRL (Shift Right Logical)
163     #10;
164     operand_a = 32'h00000004;
165     operand_b = 32'h00000001; // Shift by 1
166     alu_control = 6'b100001; // SRL
167     #10;
168     $display("SRL: 4 >> 1 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
169             operand_a, alu_result, zero, overflow, negative, carry_out);
170
171     // Test SRA (Shift Right Arithmetic)
172     #10;
173     operand_a = 32'h80000000; // Negative number
174     operand_b = 32'h00000002; // Shift by 2
175     alu_control = 6'b100010; // SRA
176     #10;
177     $display("SRA: 80000000 >> 2 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
178             operand_a, alu_result, zero, overflow, negative, carry_out);
179
180     // Test RANDOM operation (Stochastic)
181     #10;
182     alu_control = 6'b111111; // RANDOM
183     #10;
184     $display("RANDOM: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",


```

```


159     $display("SLL: 1 << 2 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
160             operand_a, alu_result, zero, overflow, negative, carry_out);
161
162     // Test SRL (Shift Right Logical)
163     #10;
164     operand_a = 32'h00000004;
165     operand_b = 32'h00000001; // Shift by 1
166     alu_control = 6'b100001; // SRL
167     #10;
168     $display("SRL: 4 >> 1 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
169             operand_a, alu_result, zero, overflow, negative, carry_out);
170
171     // Test SRA (Shift Right Arithmetic)
172     #10;
173     operand_a = 32'h80000000; // Negative number
174     operand_b = 32'h00000002; // Shift by 2
175     alu_control = 6'b100010; // SRA
176     #10;
177     $display("SRA: 80000000 >> 2 = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
178             operand_a, alu_result, zero, overflow, negative, carry_out);
179
180     // Test RANDOM operation (Stochastic)
181     #10;
182     alu_control = 6'b111111; // RANDOM
183     #10;
184     $display("RANDOM: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
185             alu_result, zero, overflow, negative, carry_out);
186
187     // Test BIT SELECT
188     #10;
189     operand_a = 32'hA5A5A5A5; // 1010 0101...
190     operand_b = 32'h00000010; // Bit 16
191     alu_control = 6'b110100; // BIT SELECT
192     #10;
193     $display("BIT SELECT: A5A5A5A5[16] = %h, Result: %h, Zero: %b, Overflow: %b, Negative: %b, Carry Out: %b",
194             operand_a, alu_result, zero, overflow, negative, carry_out);
195
196     $display("Testbench Complete");
197     $finish;
198 end
199 endmodule

```


Simulation Waveform

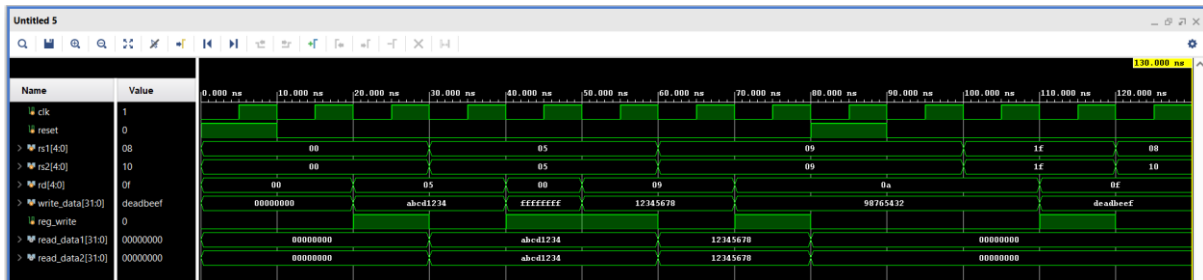

Elaborated Design

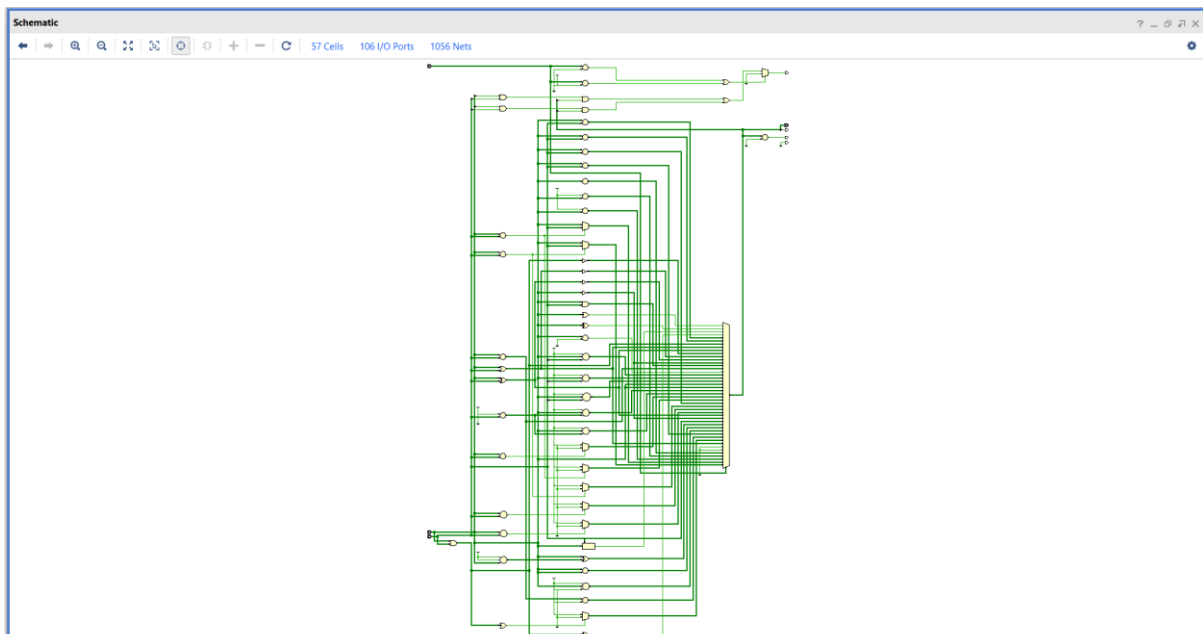

Synthesized Design

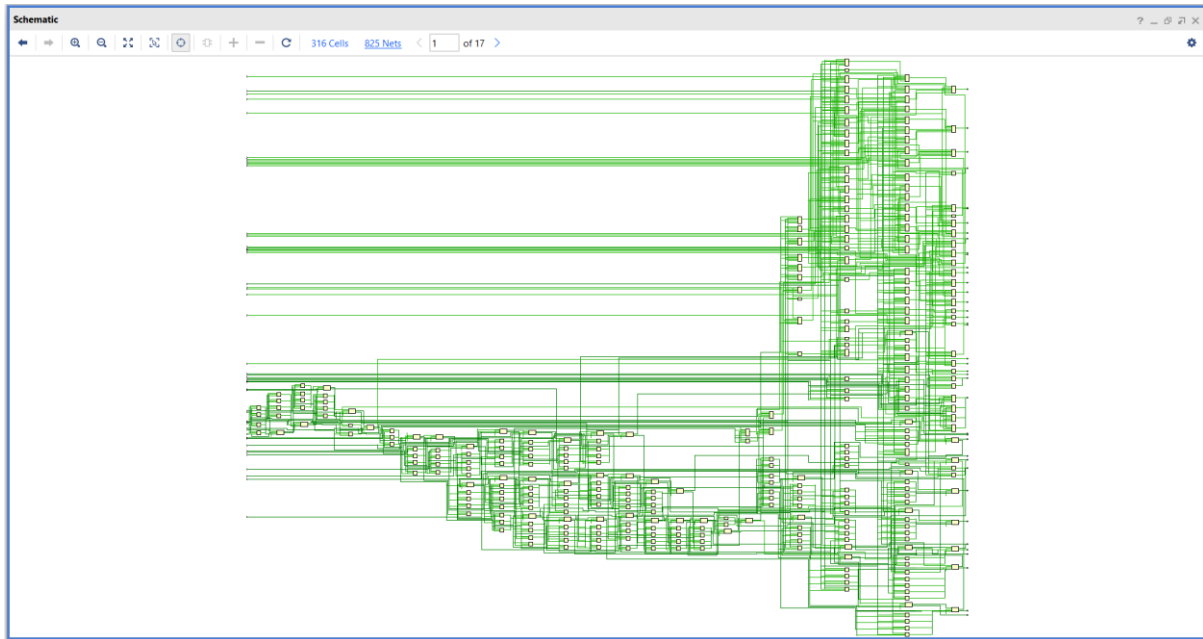

6. Module InstructionFetch

6.1 Description

The InstructionFetch module is a critical component of the RV32I Processor, responsible for fetching instructions from memory, updating the program counter (PC), and handling control flow changes such as branches, jumps, and interrupts. The design includes an instruction prefetch buffer and a simple caching mechanism to enhance instruction fetch efficiency and reduce latency.

6.2 Design Features

The InstructionFetch module includes:

1. **Instruction Fetch Logic:**
 - Fetches instructions from memory or cache based on the current PC value.
 - Uses a prefetch buffer to preload instructions and improve fetch efficiency.
2. **Program Counter (PC) Update Logic:**
 - Updates the PC based on branch, jump, interrupt signals, or sequential execution.
 - Holds the PC value during stall conditions to prevent changes.
3. **Cache Mechanism:**
 - A small cache is implemented to store recently fetched instructions, reducing memory access time.
 - Cache validation logic ensures data integrity and coherence.
4. **Prefetch Buffer:**
 - A buffer that preloads a sequence of instructions to minimize fetch latency and improve performance.
5. **Exception Handling:**
 - Detects exceptional conditions such as out-of-bounds PC values or invalid instructions.
 - Triggers an exception signal to handle errors appropriately.

6.3 Design Features

The InstructionFetch module includes:

1. **Instruction Fetch Logic:**
 - Determines whether to fetch instructions from the cache or directly from memory based on the PC value.

- Improves fetch efficiency and reduces latency.

2. PC Update Logic:

- Manages PC updates based on control signals for branching, jumping, interrupts, or normal progression.
- Holds the PC value during stall conditions.

3. Cache and Prefetch Buffer:

- Utilizes a small instruction cache and a prefetch buffer to enhance fetch performance.
- Ensures data integrity with cache validation logic.

4. Exception Detection:

- Monitors the PC and instructions to detect exceptional conditions.
- Triggers an exception signal when an error is detected.

6.4 InstructionFetch Testing (Testbench Analysis)

The tb_InstructionFetch module was designed to test and verify the functionality of the InstructionFetch module. Key points from the testbench include:

1. Initialization and Configuration:

- Initializes inputs and control signals.
- Applies reset to ensure the module starts in a known state.

2. Key Test Cases:

- **Reset Behaviour:**
 - Verifies that the PC is reset to 0 and the instruction is correctly fetched after a reset.
- **Default Instruction Fetching:**
 - Ensures correct instruction fetching during normal operation.
- **Stall Behaviour:**
 - Checks that the PC holds its value during a stall condition.
- **Branch Handling:**
 - Verifies correct PC update to the branch target when a branch is taken.
- **Jump Handling:**
 - Confirms correct PC update to the jump target when a jump is taken.
- **Interrupt Handling:**
 - Ensures correct PC update to the interrupt vector when an interrupt is taken.
- **Exception Detection:**
 - Tests the exception detection mechanism by providing invalid instructions or out-of-bounds PC values.

3. Sample Outputs:

- **Reset:**
 - PC: 0, Instruction: <initial instruction>, Exception: 0
- **Branch Taken:**
 - PC updated to branch target, Instruction: <fetched instruction>, Exception: 0
- **Jump Taken:**
 - PC updated to jump target, Instruction: <fetched instruction>, Exception: 0
- **Interrupt:**
 - PC updated to interrupt vector, Instruction: <fetched instruction>, Exception: 0

- Exception:

- PC: <out-of-bounds>, Instruction: 32'hFFFFFFF, Exception: 1

4. Results and Observations:

- All operations produced expected results under normal conditions.
- The PC correctly updated based on control signals for branches, jumps, and interrupts.
- The exception mechanism effectively detected errors and triggered the appropriate signals.
- Prefetch buffer and cache demonstrated improved fetch performance by reducing memory access times.

Verilog Code

InstructionFetch.v

D:/Vivado/RISC_1/RISC_1.srscs/sources_1/new/InstructionFetch.v

```
module InstructionFetch (
    input clk,
    input reset,
    input [31:0] branch_target,
    input branch_taken,
    input jump_taken,
    input [31:0] jump_target,
    input interrupt_taken,
    input [31:0] interrupt_vector,
    input stall,
    input [255:0] instruction_memory_input,
    output reg [31:0] pc,
    output reg [31:0] instruction,
    output reg exception
);

    reg [31:0] prefetch_buffer [0:3];
    reg [31:0] cache [0:15];
    reg cache_valid [0:15];
    integer i;

    // Instruction fetch logic
    always @(*) begin
        if (pc[31:4] < 16 && cache_valid[pc[31:4]]) begin
            instruction = cache[pc[31:4]];
        end else begin
            instruction = instruction_memory_input[(pc[6:2] * 32) +: 32];
        end
    end

    // PC update logic
    always @(posedge clk or posedge reset) begin
        if (reset) begin
            pc <= 32'b0;
        end else if (stall) begin
            pc <= pc; // Hold PC during stall
        end else if (interrupt_taken) begin
            pc <= interrupt_vector;
        end else if (branch_taken) begin
            pc <= branch_target;
        end else if (jump_taken) begin
```




```


60 initial begin
61     // Initialize inputs
62     clk = 0;
63     reset = 1;
64     branch_target = 0;
65     branch_taken = 0;
66     jump_taken = 0;
67     jump_target = 0;
68     interrupt_taken = 0;
69     interrupt_vector = 0;
70     stall = 0;
71     instruction_memory_input = {
72         32'h00000001, 32'h00000002, 32'h00000003, 32'h00000004, // First 4 instructions
73         32'h00000005, 32'h00000006, 32'h00000007, 32'h00000008, // Next 4 instructions
74         32'h00000009, 32'h0000000A, 32'h0000000B, 32'h0000000C, // Next 4 instructions
75         32'h0000000D, 32'h0000000E, 32'h0000000F, 32'h00000010 // Last 4 instructions
76     };
77     // Test 1: Reset behavior
78     #10 reset = 0;
79     #10 $display("After reset: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
80     // Test 2: Default instruction fetching
81     #10 $display("Default fetch: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
82     // Test 3: Stall behavior
83     stall = 1;
84     #20 $display("During stall: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
85     stall = 0;
86     // Test 4: Branch handling
87     branch_target = 32'h00000020;
88     branch_taken = 1;
89     #10 branch_taken = 0;
90     #10 $display("After branch: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
91     // Test 5: Jump handling
92     jump_target = 32'h00000040;
93     jump_taken = 1;
94     #10 jump_taken = 0;
95     #10 $display("After jump: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
96     // Test 6: Interrupt handling
97     interrupt_vector = 32'h00000060;
98     interrupt_taken = 1;
99     #10 interrupt_taken = 0;
100    #10 $display("After interrupt: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
101
102    32'h00000001, 32'h00000002, 32'h00000003, 32'h00000004, // First 4 instructions
103    32'h00000005, 32'h00000006, 32'h00000007, 32'h00000008, // Next 4 instructions
104    32'h00000009, 32'h0000000A, 32'h0000000B, 32'h0000000C, // Next 4 instructions
105    32'h0000000D, 32'h0000000E, 32'h0000000F, 32'h00000010 // Last 4 instructions
106
107    };
108    // Test 1: Reset behavior
109    #10 reset = 0;
110    #10 $display("After reset: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
111    // Test 2: Default instruction fetching
112    #10 $display("Default fetch: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
113    // Test 3: Stall behavior
114    stall = 1;
115    #20 $display("During stall: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
116    stall = 0;
117    // Test 4: Branch handling
118    branch_target = 32'h00000020;
119    branch_taken = 1;
120    #10 branch_taken = 0;
121    #10 $display("After branch: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
122    // Test 5: Jump handling
123    jump_target = 32'h00000040;
124    jump_taken = 1;
125    #10 jump_taken = 0;
126    #10 $display("After jump: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
127    // Test 6: Interrupt handling
128    interrupt_vector = 32'h00000060;
129    interrupt_taken = 1;
130    #10 interrupt_taken = 0;
131    #10 $display("After interrupt: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
132    // Test 7: Exception detection
133    #10 instruction_memory_input = 256'hFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFFF;
134    #10 $display("Exception case: PC=%h, Instruction=%h, Exception=%b", pc, instruction, exception);
135    // Test 8: Prefetch buffer and cache validation
136    reset = 1;
137    #10 reset = 0;
138    #10 stall = 0;
139    #50 $display("Cache and prefetch behavior test");
140    // Finish simulation
141    #100 $finish;
142 end
143 endmodule

```


Simulation Waveform

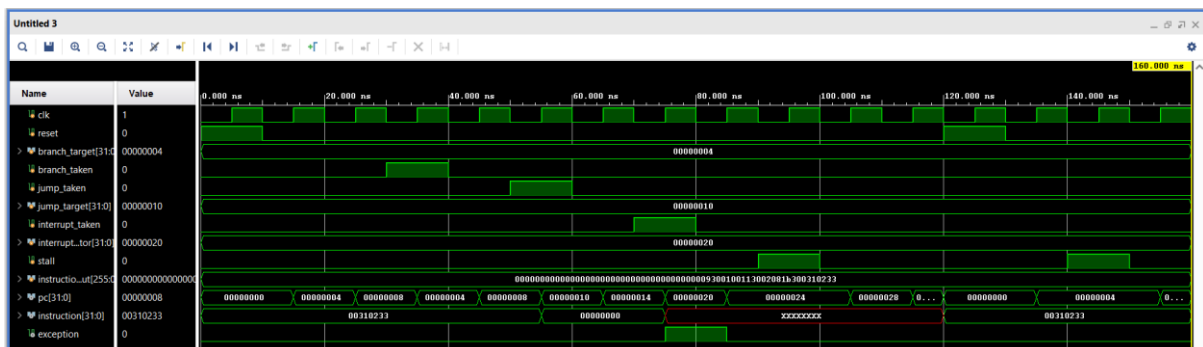

Elaborated Design

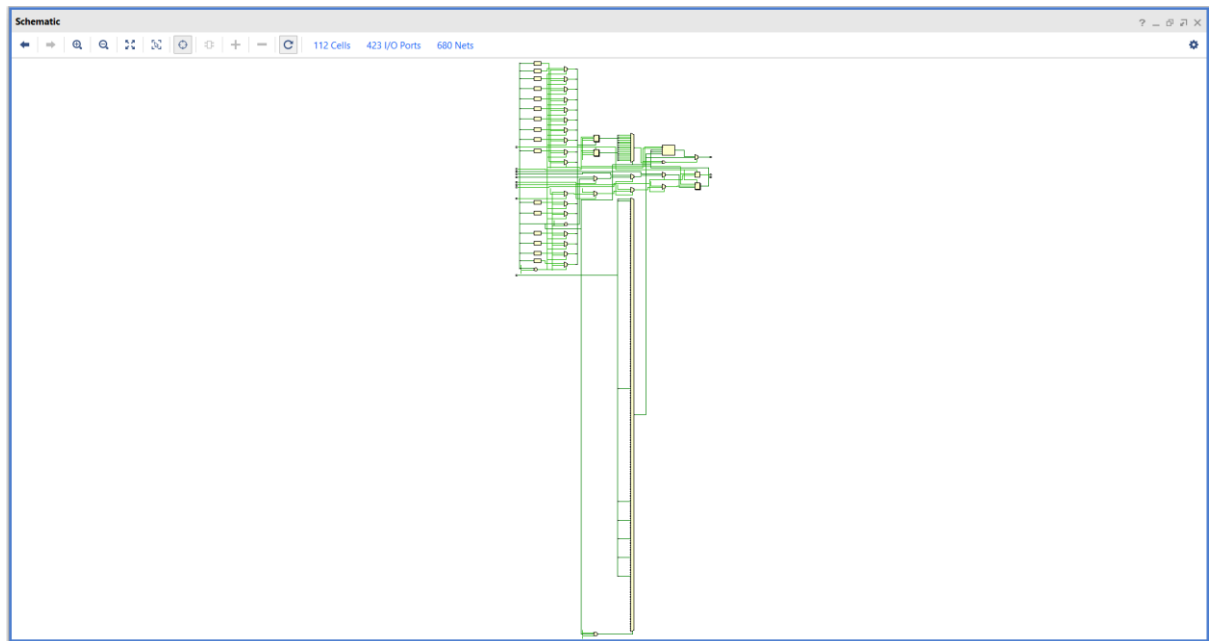

Synthesized Design

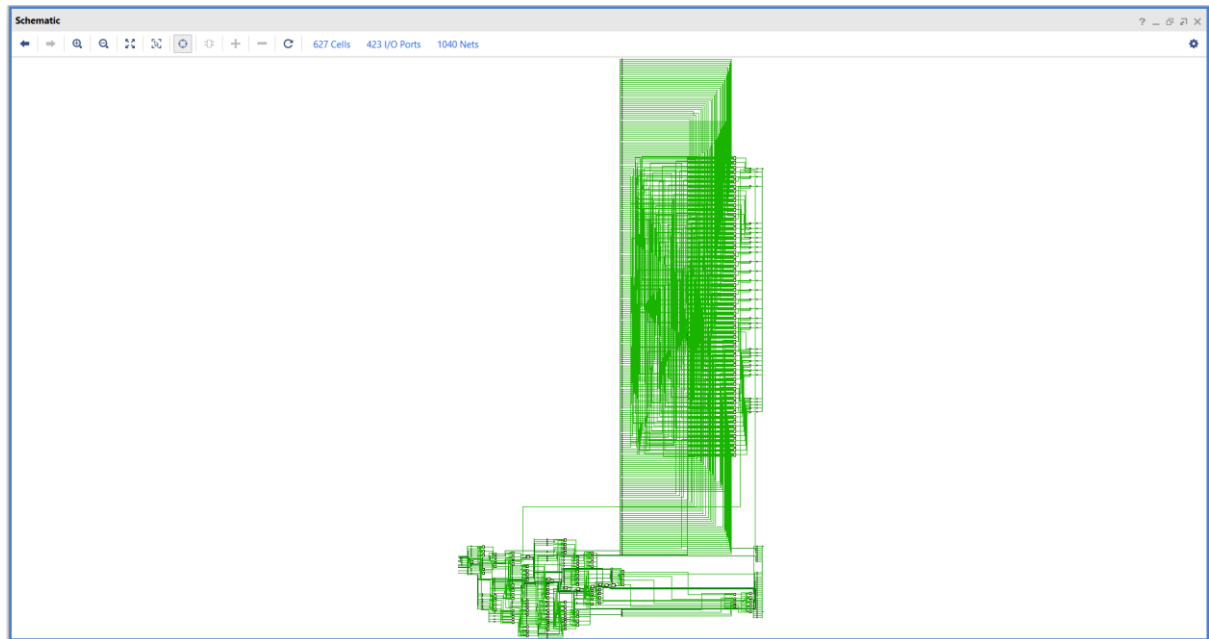

7. Module ControlUnit

7.1 Description

The ControlUnit module is a vital component of the RV32I Processor, responsible for generating control signals based on the opcode and function fields of instructions. These control signals govern the operation of various modules within the processor, enabling correct execution of instructions.

7.2 Design Features

The ControlUnit module includes:

1. Inputs:

- opcode: 7-bit opcode field that determines the type of instruction.
- funct3: 3-bit function field for R-type and I-type instructions.
- funct7: 7-bit function field for R-type instructions.

2. Outputs:

- reg_write: Enables writing to the register file.
- mem_read: Enables reading from memory.
- mem_write: Enables writing to memory.
- mem_to_reg: Selects data from memory to write back to a register.
- branch_taken: Indicates if a branch should be taken.
- imm_select: Selects immediate operand for I-type instructions.
- jump: Indicates if a jump instruction should be executed.

3. Control Signal Generation:

- Decodes the opcode and function fields to generate appropriate control signals for various instructions, including R-type, I-type, load, store, branch, and jump instructions.
- Provides default values for control signals, ensuring safe operation for undefined or unknown opcodes.

7.3 ControlUnit Testing (Testbench Analysis)

The tb_ControlUnit module was designed to test and verify the functionality of the ControlUnit module. Key points from the testbench include:

1. Initialization and Configuration:

- Initializes inputs and control signals.
- Applies various opcodes and function fields to test the generation of control signals.

2. Key Test Cases:

- **R-Type Instructions:**
 - Opcode: 7'b0110011 (e.g., ADD, SUB)
 - Verifies control signals for R-type ALU operations, ensuring correct register write and operand selection.
- **I-Type Instructions:**
 - Opcode: 7'b0010011 (e.g., ADDI)
 - Ensures correct control signal generation for immediate operations.
- **Load Instruction (lw):**
 - Opcode: 7'b0000011
 - Verifies memory read and data write-back to the register file.
- **Store Instruction (sw):**
 - Opcode: 7'b0100011
 - Ensures correct memory write operations.

- **Branch Instructions (beq):**
 - Opcode: 7'b1100011
 - Verifies branch control logic for conditional branch instructions.
- **Jump Instructions (jal, jalr):**
 - Opcodes: 7'b1101111 and 7'b1100111
 - Ensures correct PC update and register write-back for jump instructions.
- **Default Case:**
 - Tests behavior for undefined or unknown opcodes, ensuring safe default control signals.

3. Sample Outputs:

- **R-Type (ADD):**
 - reg_write=1, mem_read=0, mem_write=0, mem_to_reg=0, branch_taken=0, imm_select=0, jump=0
- **I-Type (ADDI):**
 - reg_write=1, mem_read=0, mem_write=0, mem_to_reg=0, branch_taken=0, imm_select=1, jump=0
- **Load (lw):**
 - reg_write=1, mem_read=1, mem_write=0, mem_to_reg=1, branch_taken=0, imm_select=1, jump=0
- **Store (sw):**
 - reg_write=0, mem_read=0, mem_write=1, mem_to_reg=0, branch_taken=0, imm_select=1, jump=0
- **Branch (beq):**
 - reg_write=0, mem_read=0, mem_write=0, mem_to_reg=0, branch_taken=1, imm_select=1, jump=0
- **Jump (jal):**
 - reg_write=1, mem_read=0, mem_write=0, mem_to_reg=0, branch_taken=0, imm_select=1, jump=1
- **Default:**
 - reg_write=0, mem_read=0, mem_write=0, mem_to_reg=0, branch_taken=0, imm_select=0, jump=0

4. Results and Observations:

- All control signals were generated correctly based on the opcode and function fields.
- The module correctly identified and set signals for various types of instructions, ensuring proper processor operation.
- Safe default values for control signals were provided for undefined or unknown opcodes, ensuring the processor remains stable.

Verilog Code

ControlUnit.v

D:/Vivado/RISC_1/RISC_1.srcs/sources_1/new/ControlUnit.v

```
21 module ControlUnit (
22     input [6:0] opcode,          // 7-bit opcode field
23     input [2:0] funct3,          // 3-bit funct3 field for R-type instructions
24     input [6:0] funct7,          // 7-bit funct7 field for R-type instructions
25     output reg reg_write,        // Register write signal
26     output reg mem_read,        // Memory read signal
27     output reg mem_write,       // Memory write signal
28     output reg mem_to_reg,      // Memory to register signal
29     output reg branch_taken,    // Branch taken signal
30     output reg imm_select,      // Immediate operand selection signal (I-type)
31     output reg jump,            // Jump instruction signal
32 );
33 always @(*) begin
34     // Default control signals
35     reg_write = 0;
36     mem_read = 0;
37     mem_write = 0;
38     mem_to_reg = 0;
39     branch_taken = 0;
40     imm_select = 0;
41     jump = 0;
42     case (opcode)
43         // R-Type instructions (ALU operations)
44         7'b0110011: begin // R-Type (e.g., ADD, SUB, AND, OR, etc.)
45             reg_write = 1;          // Enable writing to the register file
46             imm_select = 0;         // Use register operand (not immediate)
47             mem_read = 0;
48             mem_write = 0;
49             mem_to_reg = 0;
50             branch_taken = 0;
51             jump = 0;
52         end
53         // I-Type instructions (Immediate operations)
54         7'b0010011: begin // ADDI, SLTI, ANDI, etc.
55             reg_write = 1;
56             imm_select = 1;         // Immediate operand
57             mem_read = 0;
58             mem_write = 0;
59             mem_to_reg = 0;
60             branch_taken = 0;
61             jump = 0;
62     end
63     // Load instruction (lw)
64     7'b0000011: begin // lw
65         reg_write = 1;             // Write data from memory to register
66         mem_read = 1;             // Enable memory read
67         mem_write = 0;
68         mem_to_reg = 1;           // Load data from memory to register
69         imm_select = 1;           // Immediate address calculation
70         branch_taken = 0;
71         jump = 0;
72     end
73     // Store instruction (sw)
74     7'b0100011: begin // sw
75         reg_write = 0;            // No register write
76         mem_read = 0;
77         mem_write = 1;           // Enable memory write
78         mem_to_reg = 0;
79         imm_select = 1;           // Immediate address calculation
80         branch_taken = 0;
81         jump = 0;
82     end
83     // Branch instructions (beq, bne, etc.)
84     7'b1100011: begin // beq, bne, etc.
85         reg_write = 0;            // No register write
86         mem_read = 0;
87         mem_write = 0;
88         mem_to_reg = 0;
89         imm_select = 1;           // Immediate value for branch offset
90         branch_taken = 1;        // Enable branch logic
91         jump = 0;
92     end
93     // Jump instruction (J-Type: jal, jalr)
94     7'b1101111: begin // jal
95         reg_write = 1;            // Write PC+4 to the register
96         mem_read = 0;
97         mem_write = 0;
98         mem_to_reg = 0;
99         imm_select = 1;           // Immediate offset for jump address
100        branch_taken = 0;
101        jump = 1;                // Enable jump
102    end
end
```



```

84      7'b1100011: begin // beq, bne, etc.
85          reg_write = 0;           // No register write
86          mem_read = 0;
87          mem_write = 0;
88          mem_to_reg = 0;
89          imm_select = 1;          // Immediate value for branch offset
90          branch_taken = 1;        // Enable branch logic
91          jump = 0;
92      end
93      // Jump instruction (J-Type: jal, jalr)
94      7'b1101111: begin // jal
95          reg_write = 1;           // Write PC+4 to the register
96          mem_read = 0;
97          mem_write = 0;
98          mem_to_reg = 0;
99          imm_select = 1;          // Immediate offset for jump address
100         branch_taken = 0;
101         jump = 1;                 // Enable jump
102     end
103     7'b1100111: begin // jalr
104         reg_write = 1;           // Write the address of next instruction to register
105         mem_read = 0;
106         mem_write = 0;
107         mem_to_reg = 0;
108         imm_select = 1;          // Immediate offset for jump address
109         branch_taken = 0;
110         jump = 1;                 // Enable jump
111     end
112     // Default case (No operation)
113     default: begin
114         reg_write = 0;
115         mem_read = 0;
116         mem_write = 0;
117         mem_to_reg = 0;
118         imm_select = 0;
119         branch_taken = 0;
120         jump = 0;
121     end
122 endcase
123 end
124 endmodule

```

Testbench Code

tb_ControlUnit.v

D:/Vivado/RISC_1/RISC_1.srscs/sources_1/new/tb_ControlUnit.v

```

22 module tb_ControlUnit;
23     // Inputs to the Control Unit
24     reg [6:0] opcode;
25     reg [2:0] funct3;
26     reg [6:0] funct7;
27     // Outputs from the Control Unit
28     wire reg_write;
29     wire mem_read;
30     wire mem_write;
31     wire mem_to_reg;
32     wire branch_taken;
33     wire imm_select;
34     wire jump;
35     // Instantiate the ControlUnit module
36     ControlUnit uut (
37         .opcode(opcode),
38         .funct3(funct3),
39         .funct7(funct7),
40         .reg_write(reg_write),
41         .mem_read(mem_read),
42         .mem_write(mem_write),
43         .mem_to_reg(mem_to_reg),
44         .branch_taken(branch_taken),
45         .imm_select(imm_select),
46         .jump(jump)
47     );
48     // Test procedure
49     initial begin
50         // Apply Reset
51         $display("Starting Testbench for Control Unit");
52         // Test R-Type (e.g., ADD)
53         opcode = 7'b0110011; // R-Type opcode
54         funct3 = 3'b000;      // ADD funct3
55         funct7 = 7'b0000000;  // No special funct7 for ADD
56         #10;
57         $display("R-Type (ADD): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
58             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
59         // Test I-Type (e.g., ADDI)
60         opcode = 7'b0010011; // I-Type opcode
61         funct3 = 3'b000;      // ADDI funct3
62         funct7 = 7'b0000000;  // No funct7 for ADDI


```

```


63     #10;
64     $display("I-Type (ADDI): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
65             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
66     // Test Load instruction (lw)
67     opcode = 7'b0000011; // Load opcode (lw)
68     funct3 = 3'b010; // lw funct3
69     funct7 = 7'b0000000; // No funct7 for lw
70     #10;
71     $display("Load (lw): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
72             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
73     // Test Store instruction (sw)
74     opcode = 7'b0100011; // Store opcode (sw)
75     funct3 = 3'b010; // sw funct3
76     funct7 = 7'b0000000; // No funct7 for sw
77     #10;
78     $display("Store (sw): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
79             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
80     // Test Branch instruction (beq)
81     opcode = 7'b1100011; // Branch opcode (beq)
82     funct3 = 3'b000; // beq funct3
83     funct7 = 7'b0000000; // No funct7 for beq
84     #10;
85     $display("Branch (beq): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
86             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
87     // Test Jump instruction (jal)
88     opcode = 7'b1101111; // Jump opcode (jal)
89     funct3 = 3'b000; // No funct3 for jal
90     funct7 = 7'b0000000; // No funct7 for jal
91     #10;
92     $display("Jump (jal): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
93             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
94     // Test Jump and Link Register instruction (jalr)
95     opcode = 7'b1100111; // Jump opcode (jalr)
96     funct3 = 3'b000; // No funct3 for jalr
97     funct7 = 7'b0000000; // No funct7 for jalr
98     #10;
99     $display("Jump and Link Register (jalr): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
100             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
101     // Test default (Unknown opcode)
102     opcode = 7'b1111111; // Unknown opcode
103     funct3 = 3'b111; // Random funct3
104
105     #10;
106     $display("Load (lw): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
107             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
108     // Test Store instruction (sw)
109     opcode = 7'b0100011; // Store opcode (sw)
110     funct3 = 3'b010; // sw funct3
111     funct7 = 7'b0000000; // No funct7 for sw
112     #10;
113     $display("Store (sw): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
114             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
115     // Test Branch instruction (beq)
116     opcode = 7'b1100011; // Branch opcode (beq)
117     funct3 = 3'b000; // beq funct3
118     funct7 = 7'b0000000; // No funct7 for beq
119     #10;
120     $display("Branch (beq): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
121             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
122     // Test Jump instruction (jal)
123     opcode = 7'b1101111; // Jump opcode (jal)
124     funct3 = 3'b000; // No funct3 for jal
125     funct7 = 7'b0000000; // No funct7 for jal
126     #10;
127     $display("Jump (jal): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
128             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
129     // Test Jump and Link Register instruction (jalr)
130     opcode = 7'b1100111; // Jump opcode (jalr)
131     funct3 = 3'b000; // No funct3 for jalr
132     funct7 = 7'b0000000; // No funct7 for jalr
133     #10;
134     $display("Jump and Link Register (jalr): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
135             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
136     // Test default (Unknown opcode)
137     opcode = 7'b1111111; // Unknown opcode
138     funct3 = 3'b111; // Random funct3
139     funct7 = 7'b1111111; // Random funct7
140     #10;
141     $display("Default (Unknown opcode): reg_write=%b, mem_read=%b, mem_write=%b, mem_to_reg=%b, branch_taken=%b, imm_select=%b, jump=%b",
142             reg_write, mem_read, mem_write, mem_to_reg, branch_taken, imm_select, jump);
143     $stop;
144 end
145 endmodule

```


Simulation Waveform

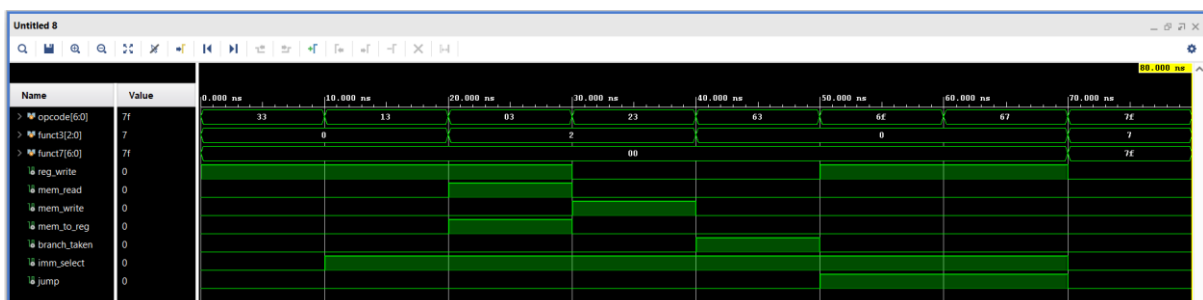

Elaborated Design

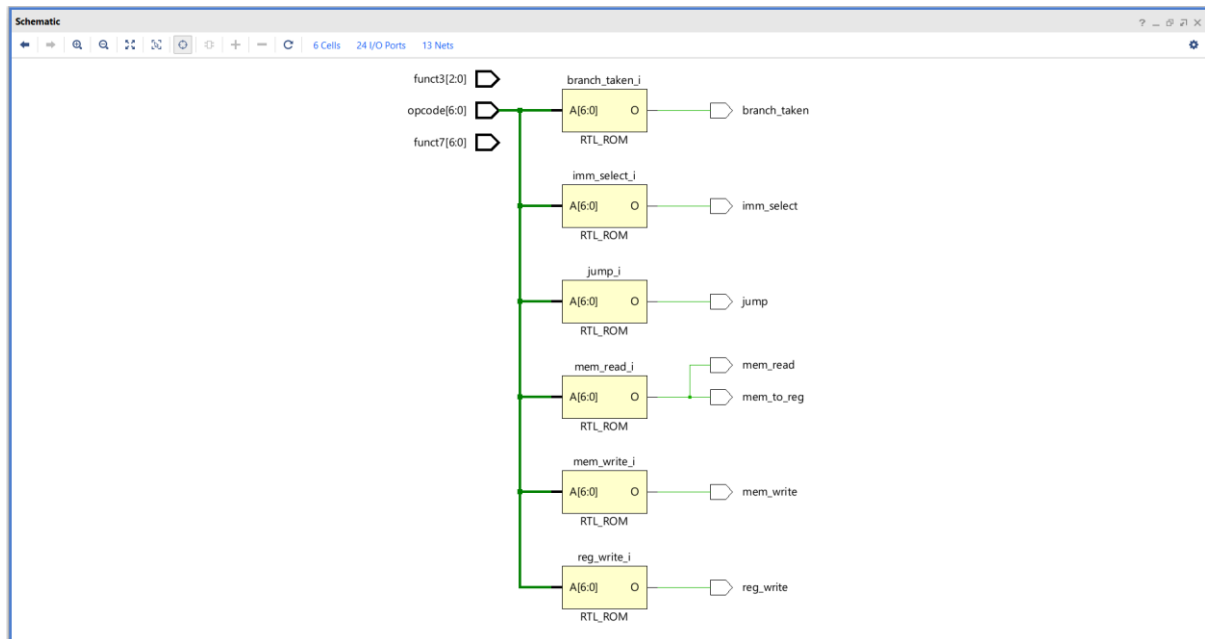

Synthesized Design

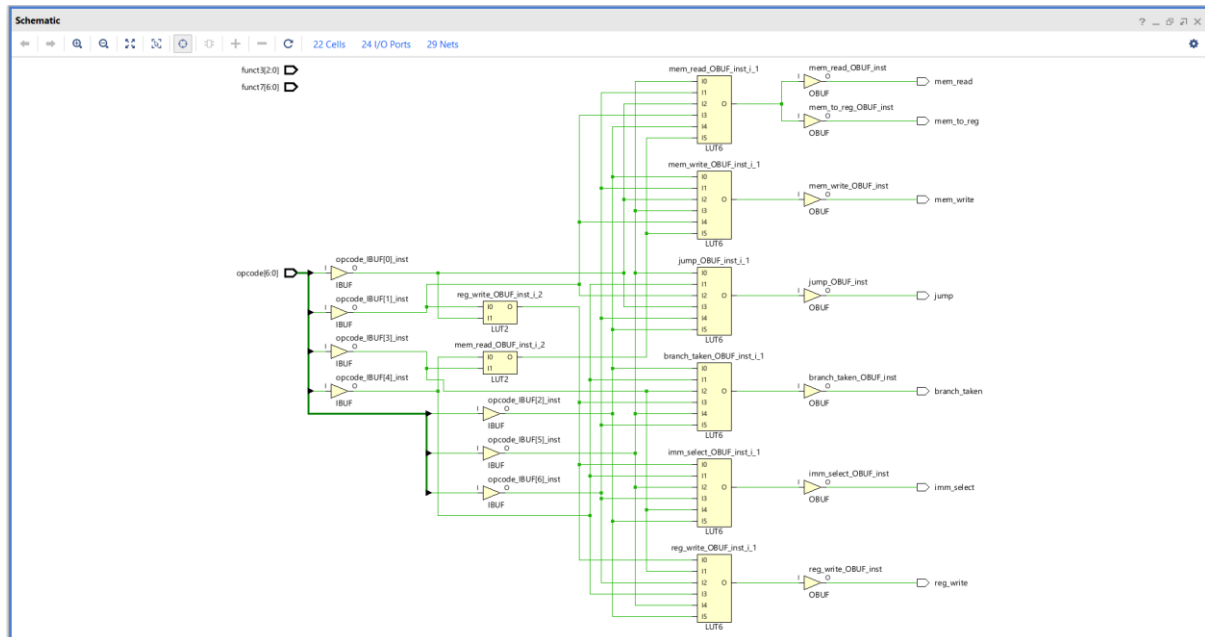

8. Module RegisterFile

8.1 Description

The RegisterFile module is a crucial component of the RV32I Processor, providing storage for the processor's general-purpose registers. It allows reading from two registers and writing to one register in a single clock cycle, facilitating efficient instruction execution. The design includes features to ensure data integrity and proper operation under various conditions.

8.2 Design Features

The RegisterFile module includes:

1. Inputs:

- clk: Clock signal.
- reset: Reset signal to clear all registers.
- rs1: 5-bit address for the first read register.
- rs2: 5-bit address for the second read register.
- rd: 5-bit address for the write register.
- write_data: 32-bit data to be written to the register addressed by rd.
- reg_write: Write enable signal.

2. Outputs:

- read_data1: 32-bit data read from the register addressed by rs1.
- read_data2: 32-bit data read from the register addressed by rs2.

3. Register Array:

- An array of 32 registers, each 32 bits wide, providing storage for the processor's general-purpose registers.
- Register 0 is hardwired to 0, ensuring it always holds the value 0.

4. Control Logic:

- Implements asynchronous reset to clear all registers when the reset signal is active.
- Allows writing to any register except register 0, ensuring that register 0 always holds 0.
- Supports simultaneous reading from two registers.

8.3 RegisterFile Testing (Testbench Analysis)

The tb_RegisterFile module was designed to test and verify the functionality of the RegisterFile module. Key points from the testbench include:

1. Initialization and Configuration:

- Initializes inputs and control signals.
- Applies reset to ensure all registers are cleared.

2. Key Test Cases:

- **Reset Behaviour:**
 - Verifies that all registers are cleared after a reset operation.
- **Write and Read Operations:**
 - Tests writing to a register and reading from the same register to ensure correct data storage and retrieval.
- **Write to Register 0:**
 - Ensures that writes to register 0 are ignored and the register remains 0.
- **Multiple Register Operations:**
 - Verifies writing and reading from multiple registers to ensure correct operation.

- **Reset After Write:**
 - Ensures that data written to registers are cleared after a reset operation.
- **Read Uninitialized Register:**
 - Verifies that uninitialized registers return 0.
- **Effect on Other Registers:**
 - Ensures writing to one register does not affect other registers.

3. Sample Outputs:

- **Reset:**
 - Registers cleared after reset: All registers hold 0.
- **Write and Read:**
 - Writing 0xABCD1234 to register 5 and reading from the same register produces the correct data.
- **Write to Register 0:**
 - Register 0 remains 0 after attempted write.
- **Multiple Registers:**
 - Writing to register 9 and reading the correct data from the same register.
- **Reset After Write:**
 - Data in registers are cleared after reset.
- **Uninitialized Registers:**
 - Uninitialized registers return 0 when read.
- **Effect on Other Registers:**
 - Writing to one register does not affect other registers.

4. Results and Observations:

- All tests produced expected results, demonstrating correct operation of the RegisterFile module.
- The register file correctly handled reads and writes, maintained data integrity, and adhered to the design specifications.
- The reset functionality effectively cleared all registers, ensuring a known state for the processor.
- Writing to register 0 was ignored, ensuring it always held the value 0.

Verilog Code

RegisterFile.v

D:/Vivado/RISC_1/RISC_1.srcs/sources_1/new/RegisterFile.v

```
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21
22 module RegisterFile (
23     input clk,
24     input reset,
25     input [4:0] rs1,      // Register address for read data 1
26     input [4:0] rs2,      // Register address for read data 2
27     input [4:0] rd,       // Register address for write data
28     input [31:0] write_data, // Data to be written to register rd
29     input reg_write,      // Write enable signal
30     output [31:0] read_data1, // Read data from register rs1
31     output [31:0] read_data2 // Read data from register rs2
32 );
33
34 // Register file array of 32 registers, each 32 bits wide
35 reg [31:0] registers [0:31];
36 // Integer variable for loop (reset logic)
37 integer i;
38 // Asynchronous reset block: Clears all registers to 0
39 always @(posedge clk or posedge reset) begin
40     if (reset) begin
41         // Clear all registers when reset is active
42         for (i = 0; i < 32; i = i + 1) begin
43             registers[i] <= 32'b0;
44         end
45     end else if (reg_write && rd != 5'b0) begin
46         // Write to register rd, but prevent write to register 0 (it's always 0)
47         registers[rd] <= write_data;
48     end
49 end
50 // Simultaneous read from register file
51 assign read_data1 = registers[rs1]; // Read from register rs1
52 assign read_data2 = registers[rs2]; // Read from register rs2
53
54 endmodule
```

Testbench Code

tb_RegisterFile.v

D:/Vivado/RISC_1/RISC_1.srcs/sources_1/new/tb_RegisterFile.v

```
22 module tb_RegisterFile;
23
24     // Testbench signals
25     reg clk;
26     reg reset;
27     reg [4:0] rs1, rs2, rd;
28     reg [31:0] write_data;
29     reg reg_write;
30     wire [31:0] read_data1, read_data2;
31
32     // Instantiate the RegisterFile module
33     RegisterFile uut (
34         .clk(clk),
35         .reset(reset),
36         .rs1(rs1),
37         .rs2(rs2),
38         .rd(rd),
39         .write_data(write_data),
40         .reg_write(reg_write),
41         .read_data1(read_data1),
42         .read_data2(read_data2)
43     );
44     // Clock generation
45     always begin
46         #5 clk = ~clk; // Toggle clock every 5 ns
47     end
48     // Test procedure
49     initial begin
50         // Initialize signals
51         clk = 0;
52         reset = 0;
53         rs1 = 5'b0;
54         rs2 = 5'b0;
55         rd = 5'b0;
56         write_data = 32'b0;
57         reg_write = 0;
58         // Test 1: Reset test - Ensure all registers are cleared
59         $display("Test 1: Reset Test");
60         reset = 1;
61         #10;
62         reset = 0;
```

```

63     #10;
64     if (uut.registers[0] !== 32'b0 || uut.registers[1] !== 32'b0) begin
65         $display("ERROR: Registers are not cleared after reset.");
66     end else begin
67         $display("PASS: Registers cleared after reset.");
68     end
69     // Test 2: Writing and reading a register (Write to rd[5] and read from rs1[5] and rs2[5])
70     $display("\nTest 2: Write and Read Test");
71     rd = 5'b00101; // Register 5
72     write_data = 32'hABCD1234; // Data to write
73     reg_write = 1; // Enable write
74     #10;
75     reg_write = 0; // Disable write
76     // Read from the same register
77     rs1 = 5'b00101; // Register 5 for read
78     rs2 = 5'b00101; // Register 5 for read
79     #10;
80     if (read_data1 !== 32'hABCD1234 || read_data2 !== 32'hABCD1234) begin
81         $display("ERROR: Incorrect data read from register 5.");
82     end else begin
83         $display("PASS: Correct data read from register 5.");
84     end
85     // Test 3: Writing to register 0 (should not write)
86     $display("\nTest 3: Write to Register 0");
87     rd = 5'b00000; // Register 0 (Read-Only)
88     write_data = 32'hFFFFFFF; // Attempt to write 0xFFFFFFFF
89     reg_write = 1; // Enable write
90     #10;
91     reg_write = 0; // Disable write
92     // Verify register 0 still holds 0
93     if (uut.registers[0] !== 32'b0) begin
94         $display("ERROR: Register 0 should remain 0.");
95     end else begin
96         $display("PASS: Register 0 remains 0.");
97     end
98     // Test 4: Writing and reading multiple registers
99     $display("\nTest 4: Multiple Registers Test");
100    rd = 5'b01001; // Register 9
101    write_data = 32'h12345678; // Data to write
102    reg_write = 1;
103    #10;

```

```

104    reg_write = 0;
105    rs1 = 5'b01001; // Read from register 9
106    rs2 = 5'b01001; // Read from register 9
107    #10;
108    if (read_data1 !== 32'h12345678 || read_data2 !== 32'h12345678) begin
109        $display("ERROR: Incorrect data read from register 9.");
110    end else begin
111        $display("PASS: Correct data read from register 9.");
112    end
113    // Test 5: Reset after write (ensure write does not persist after reset)
114    $display("\nTest 5: Reset after Write");
115    rd = 5'b01010; // Register 10
116    write_data = 32'h98765432; // Data to write
117    reg_write = 1;
118    #10;
119    reg_write = 0;
120    reset = 1; // Trigger reset
121    #10;
122    reset = 0; // Release reset
123    #10;
124    if (uut.registers[10] !== 32'b0) begin
125        $display("ERROR: Data in register 10 should be cleared after reset.");
126    end else begin
127        $display("PASS: Data in register 10 cleared after reset.");
128    end
129    // Test 6: Edge case - Read from an uninitialized register
130    $display("\nTest 6: Read Uninitialized Register");
131    rs1 = 5'b11111; // Register 31 (uninitialized)
132    rs2 = 5'b11111; // Register 31 (uninitialized)
133    #10;
134    if (read_data1 !== 32'b0 || read_data2 !== 32'b0) begin
135        $display("ERROR: Uninitialized registers should return 0.");
136    end else begin
137        $display("PASS: Uninitialized registers return 0.");
138    end
139    // Test 7: Writing to a register and ensuring other registers are unaffected
140    $display("\nTest 7: Writing to One Register and Checking Others");
141    rd = 5'b01111; // Register 15
142    write_data = 32'hDEADBEEF; // Data to write
143    reg_write = 1;
144    #10;


```

```


118     #10;
119     reg_write = 0;
120     reset = 1; // Trigger reset
121     #10;
122     reset = 0; // Release reset
123     #10;
124     if (uut.registers[10] !== 32'b0) begin
125         $display("ERROR: Data in register 10 should be cleared after reset.");
126     end else begin
127         $display("PASS: Data in register 10 cleared after reset.");
128     end
129     // Test 6: Edge case - Read from an uninitialized register
130     $display("\nTest 6: Read Uninitialized Register");
131     rs1 = 5'b11111; // Register 31 (uninitialized)
132     rs2 = 5'b11111; // Register 31 (uninitialized)
133     #10;
134     if (read_data1 !== 32'b0 || read_data2 !== 32'b0) begin
135         $display("ERROR: Uninitialized registers should return 0.");
136     end else begin
137         $display("PASS: Uninitialized registers return 0.");
138     end
139     // Test 7: Writing to a register and ensuring other registers are unaffected
140     $display("\nTest 7: Writing to One Register and Checking Others");
141     rd = 5'b01111; // Register 15
142     write_data = 32'hDEADBEEF; // Data to write
143     reg_write = 1;
144     #10;
145     reg_write = 0;
146     // Read from other registers
147     rs1 = 5'b01000; // Register 8
148     rs2 = 5'b10000; // Register 16
149     #10;
150     if (read_data1 !== 32'b0 || read_data2 !== 32'b0) begin
151         $display("ERROR: Registers 8 and 16 should not be affected by write to register 15.");
152     end else begin
153         $display("PASS: Registers 8 and 16 unaffected by write to register 15.");
154     end
155     $display("\nAll tests completed.");
156     $finish;
157 end
158 endmodule

```


Simulation Waveform

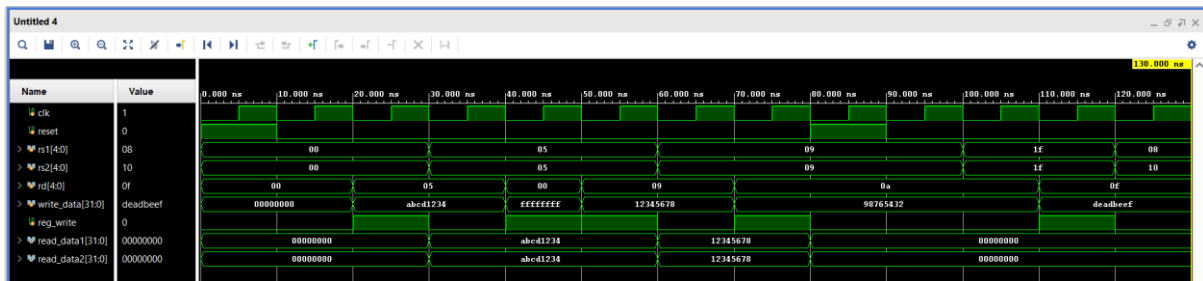

Elaborated Design

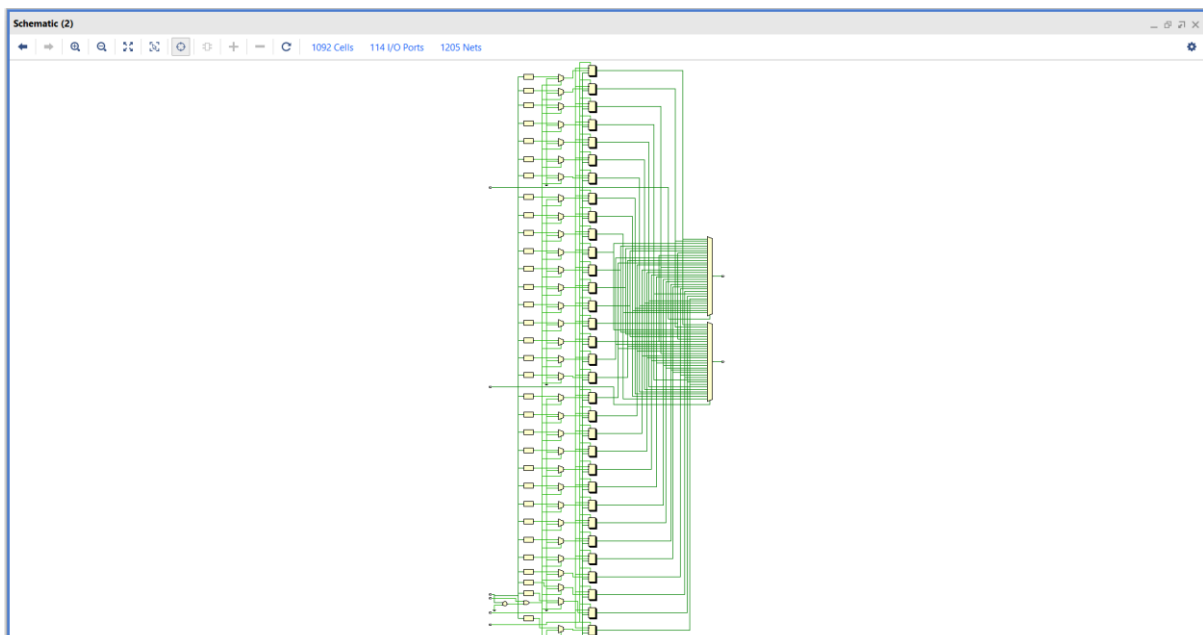


Synthesized Design

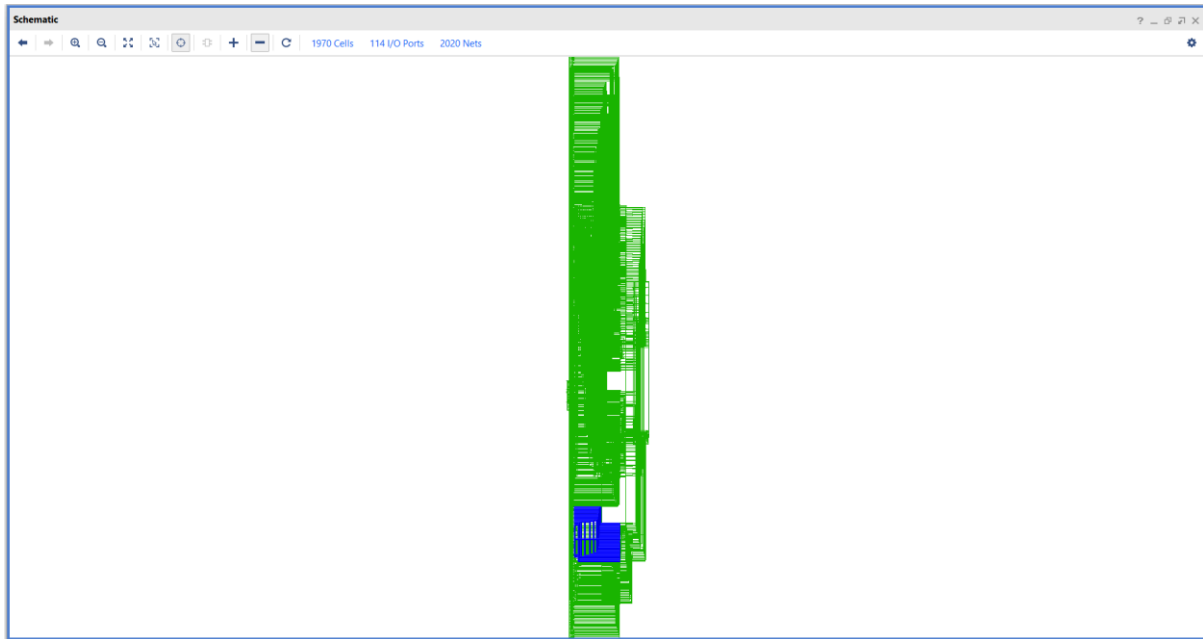

9. Implementation and Placement Errors

During the implementation and placement phase of the RV32I Processor design, several errors were encountered due to I/O overutilization and placement failures. Below is a detailed analysis of these issues and recommendations for rectification.

9.1 I/O Overutilization

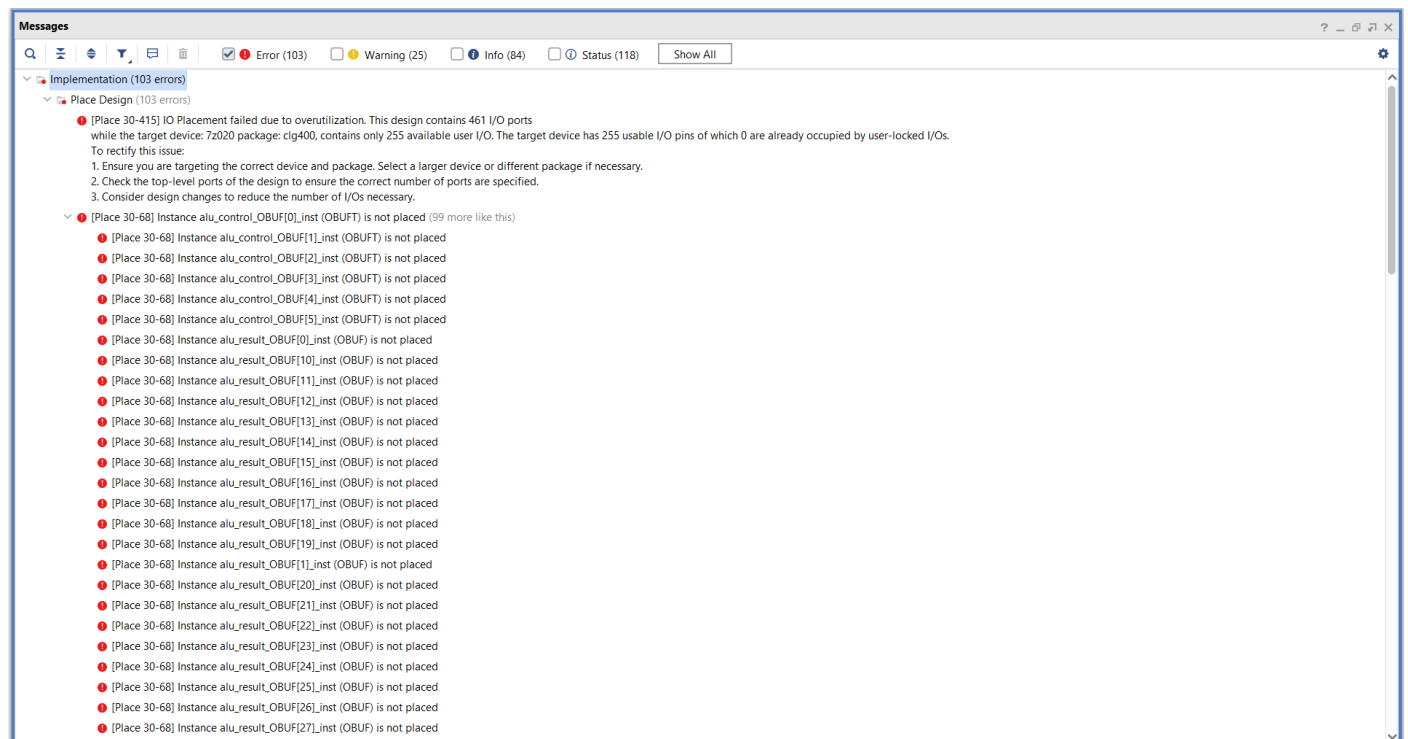

Analysis: The RV32I Processor design currently includes 461 I/O ports, which exceeds the 255 available user I/O pins on the target device (7z020, package: clg400). This overutilization prevents the successful placement of the design on the FPGA.

Recommendations:

1. Targeting the Correct Device:

- Verify that the correct device and package are being targeted for the design.
- If necessary, select a larger device or a different package that provides more I/O pins.

2. Top-Level Ports:

- Review the top-level ports of the design to ensure that the specified number of ports matches the requirements.

3. Design Changes:

- Consider design changes to reduce the number of I/O ports. This could include consolidating signals or using serial communication methods to minimize I/O usage.

9.2 Placement Failures

Analysis: Several instances of output buffers (OBUF), input buffers (IBUF), and clock buffers (BUFG) failed to be placed. This issue is a direct consequence of the I/O overutilization problem, as the design exceeds the available I/O resources on the target FPGA.

Recommendations:

1. Reevaluate the I/O Usage:

- Reduce the number of I/O ports used in the design to fit within the constraints of the target device.

2. Optimize Placement:

- Ensure that critical instances such as clock buffers (BUFG) are prioritized during placement to avoid clock-related issues.

3. Review Design Constraints:

- Check and modify design constraints to improve the placement of instances. This may involve adjusting the floorplan or placement directives.

9.3 Overall Recommendations

1. Verify Device and Package:

- Ensure the selected device and package meet the I/O requirements of the design. Consider using a device with a larger I/O capacity if the current selection is insufficient.

2. Review and Optimize Top-Level Ports:

- Assess the top-level design to confirm the number of ports. Aim to minimize I/O usage by optimizing the design.

3. Design Adjustments:

- Implement design changes such as signal consolidation or serial communication to reduce the number of required I/O ports.

4. Placement Optimization:

- Prioritize critical instances during placement, especially clock buffers, to ensure stable operation.

5. Thorough Review of Constraints and Warnings:

- Regularly review all error, warning, and critical warning messages during the design process to address issues promptly and effectively.

10. Error Report and Analysis

The design implementation encountered several errors during the "Place Design" phase. Key issues included:

- **IO Placement Overutilization:** The design contains 461 I/O ports, exceeding the 255 usable I/O pins available on the target device (7z020, package: clg400). This overutilization led to placement failures, where many I/O buffers (OBUFs) could not be placed.
 - **Error Detail:** The report lists numerous instances of OBUF placement failures, indicating that the design exceeds the I/O capacity of the FPGA device.

11. Conclusion

The RV32I Processor project demonstrates the importance of balancing design complexity with hardware constraints. Addressing the I/O placement issues will be crucial for successful implementation. The design and testing of this processor provide valuable insights into the challenges and solutions in digital IC design, offering a solid foundation for future projects.

This report covers the essential aspects of the RV32I Processor design, including module descriptions, error analysis, and recommendations for improvement.